

**P20.29** (a)  $E = \boxed{0}$  ;

$$V = \frac{k_e q}{R} = \frac{(8.99 \times 10^9)(26.0 \times 10^{-6})}{0.140} = \boxed{1.67 \text{ MV}}$$

(b)  $E = \frac{k_e q}{r^2} = \frac{(8.99 \times 10^9)(26.0 \times 10^{-6})}{(0.200)^2} = \boxed{5.84 \text{ MN/C}}$  away

$$V = \frac{k_e q}{R} = \frac{(8.99 \times 10^9)(26.0 \times 10^{-6})}{0.200} = \boxed{1.17 \text{ MV}}$$

(c)  $E = \frac{k_e q}{R^2} = \frac{(8.99 \times 10^9)(26.0 \times 10^{-6})}{(0.140)^2} = \boxed{11.9 \text{ MN/C}}$  away

$$V = \frac{k_e q}{R} = \boxed{1.67 \text{ MV}}$$

**P20.30** (a) Both spheres must be at the same potential according to  $\frac{k_e q_1}{r_1} = \frac{k_e q_2}{r_2}$

where also  $q_1 + q_2 = 1.20 \times 10^{-6} \text{ C}$  .

Then  $q_1 = \frac{q_2 r_1}{r_2}$

$$\frac{q_2 r_1}{r_2} + q_2 = 1.20 \times 10^{-6} \text{ C}$$

$$q_2 = \frac{1.20 \times 10^{-6} \text{ C}}{1 + 6 \text{ cm}/2 \text{ cm}} = 0.300 \times 10^{-6} \text{ C on the smaller sphere}$$

$$q_1 = 1.20 \times 10^{-6} \text{ C} - 0.300 \times 10^{-6} \text{ C} = 0.900 \times 10^{-6} \text{ C}$$

$$V = \frac{k_e q_1}{r_1} = \frac{(8.99 \times 10^9 \text{ N} \cdot \text{m}^2/\text{C}^2)(0.900 \times 10^{-6} \text{ C})}{6 \times 10^{-2} \text{ m}} = \boxed{1.35 \times 10^5 \text{ V}}$$

*continued on next page*

(b) Outside the larger sphere,

$$\vec{E}_1 = \frac{k_e q_1}{r_1^2} \hat{r} = \frac{V_1}{r_1} \hat{r} = \frac{1.35 \times 10^5 \text{ V}}{0.06 \text{ m}} \hat{r} = \boxed{2.25 \times 10^6 \text{ V/m away}}.$$

Outside the smaller sphere,

$$\vec{E}_2 = \frac{1.35 \times 10^5 \text{ V}}{0.02 \text{ m}} \hat{r} = \boxed{6.74 \times 10^6 \text{ V/m away}}.$$

The smaller sphere carries less charge but creates a much stronger electric field than the larger sphere.

**P20.31** (a)  $Q = C\Delta V = (4.00 \times 10^{-6} \text{ F})(12.0 \text{ V}) = 4.80 \times 10^{-5} \text{ C} = \boxed{48.0 \mu\text{C}}$

(b)  $Q = C\Delta V = (4.00 \times 10^{-6} \text{ F})(1.50 \text{ V}) = 6.00 \times 10^{-6} \text{ C} = \boxed{6.00 \mu\text{C}}$

**P20.35** (a)  $\Delta V = Ed$

$$E = \frac{20.0 \text{ V}}{1.80 \times 10^{-3} \text{ m}} = \boxed{11.1 \text{ kV/m}}$$

(b)  $E = \frac{\sigma}{\epsilon_0}$

$$\sigma = (1.11 \times 10^4 \text{ N/C})(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2) = \boxed{98.3 \text{ nC/m}^2}$$

(c)  $C = \frac{\epsilon_0 A}{d} = \frac{(8.85 \times 10^{-12} \text{ C}^2/\text{N} \cdot \text{m}^2)(7.60 \text{ cm}^2)(1.00 \text{ m}/100 \text{ cm})^2}{1.80 \times 10^{-3} \text{ m}} = \boxed{3.74 \text{ pF}}$

(d)  $\Delta V = \frac{Q}{C}$

$$Q = (20.0 \text{ V})(3.74 \times 10^{-12} \text{ F}) = \boxed{74.7 \text{ pC}}$$

**P20.36** (a)  $C = \frac{\ell}{2k_e \ln\left(\frac{b}{a}\right)} = \frac{50.0}{2(8.99 \times 10^9) \ln\left(\frac{7.27}{2.58}\right)} = \boxed{2.68 \text{ nF}}$

(b) Method 1:  $\Delta V = 2k_e \lambda \ln\left(\frac{b}{a}\right)$

$$\lambda = \frac{q}{\ell} = \frac{8.10 \times 10^{-6} \text{ C}}{50.0 \text{ m}} = 1.62 \times 10^{-7} \text{ C/m}$$

$$\Delta V = 2(8.99 \times 10^9)(1.62 \times 10^{-7}) \ln\left(\frac{7.27}{2.58}\right) = \boxed{3.02 \text{ kV}}$$

Method 2:  $\Delta V = \frac{Q}{C} = \frac{8.10 \times 10^{-6}}{2.68 \times 10^{-9}} = \boxed{3.02 \text{ kV}}$

- P20.39** (a) Capacitors in parallel add. Thus, the equivalent capacitor has a value of

$$C_{eq} = C_1 + C_2 = 5.00 \mu\text{F} + 12.0 \mu\text{F} = \boxed{17.0 \mu\text{F}} .$$

- (b) The potential difference across each branch is the same and equal to the voltage of the battery.

$$\Delta V = \boxed{9.00 \text{ V}}$$

- (c)  $Q_5 = C\Delta V = (5.00 \mu\text{F})(9.00 \text{ V}) = \boxed{45.0 \mu\text{C}}$

and  $Q_{12} = C\Delta V = (12.0 \mu\text{F})(9.00 \text{ V}) = \boxed{108 \mu\text{C}}$

**P20.40** (a) In series capacitors add as

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{5.00 \mu\text{F}} + \frac{1}{12.0 \mu\text{F}}$$

and

$$C_{eq} = \boxed{3.53 \mu\text{F}} .$$

(c) The charge on the equivalent capacitor is

$$Q_{eq} = C_{eq} \Delta V = (3.53 \mu\text{F})(9.00 \text{ V}) = 31.8 \mu\text{C} .$$

Each of the series capacitors has this same charge on it.

So

$$Q_1 = Q_2 = \boxed{31.8 \mu\text{C}} .$$

(b) The potential difference across each is

$$\Delta V_1 = \frac{Q_1}{C_1} = \frac{31.8 \mu\text{C}}{5.00 \mu\text{F}} = \boxed{6.35 \text{ V}}$$

and

$$\Delta V_2 = \frac{Q_2}{C_2} = \frac{31.8 \mu\text{C}}{12.0 \mu\text{F}} = \boxed{2.65 \text{ V}}$$

**P20.41** (a)  $\frac{1}{C_s} = \frac{1}{15.0} + \frac{1}{3.00}$

$$C_s = 2.50 \mu\text{F}$$

$$C_p = 2.50 + 6.00 = 8.50 \mu\text{F}$$

$$C_{eq} = \left( \frac{1}{8.50 \mu\text{F}} + \frac{1}{20.0 \mu\text{F}} \right)^{-1} = \boxed{5.96 \mu\text{F}}$$


(b)  $Q = C \Delta V = (5.96 \mu\text{F})(15.0 \text{ V}) = \boxed{89.5 \mu\text{C}}$  on  $20.0 \mu\text{F}$

$$\Delta V = \frac{Q}{C} = \frac{89.5 \mu\text{C}}{20.0 \mu\text{F}} = 4.47 \text{ V}$$

$$15.0 - 4.47 = 10.53 \text{ V}$$

$$Q = C \Delta V = (6.00 \mu\text{F})(10.53 \text{ V}) = \boxed{63.2 \mu\text{C}}$$
 on  $6.00 \mu\text{F}$

$$89.5 - 63.2 = \boxed{26.3 \mu\text{C}}$$
 on  $15.0 \mu\text{F}$  and  $3.00 \mu\text{F}$

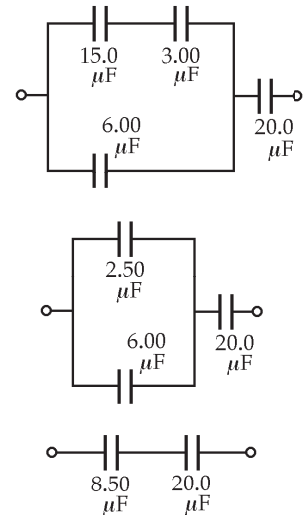

**FIG. P20.41**

**P20.39** (a) Capacitors in parallel add. Thus, the equivalent capacitor has a value of

$$C_{eq} = C_1 + C_2 = 5.00 \mu\text{F} + 12.0 \mu\text{F} = \boxed{17.0 \mu\text{F}} .$$

- (b) The potential difference across each branch is the same and equal to the voltage of the battery.

$$\Delta V = \boxed{9.00 \text{ V}}$$

(c)  $Q_5 = C\Delta V = (5.00 \mu\text{F})(9.00 \text{ V}) = \boxed{45.0 \mu\text{C}}$

and  $Q_{12} = C\Delta V = (12.0 \mu\text{F})(9.00 \text{ V}) = \boxed{108 \mu\text{C}}$

**P20.40** (a) In series capacitors add as

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{5.00 \mu\text{F}} + \frac{1}{12.0 \mu\text{F}}$$

and

$$C_{eq} = \boxed{3.53 \mu\text{F}} .$$

(c) The charge on the equivalent capacitor is

$$Q_{eq} = C_{eq} \Delta V = (3.53 \mu\text{F})(9.00 \text{ V}) = 31.8 \mu\text{C} .$$

Each of the series capacitors has this same charge on it.

So

$$Q_1 = Q_2 = \boxed{31.8 \mu\text{C}} .$$

(b) The potential difference across each is

$$\Delta V_1 = \frac{Q_1}{C_1} = \frac{31.8 \mu\text{C}}{5.00 \mu\text{F}} = \boxed{6.35 \text{ V}}$$

and

$$\Delta V_2 = \frac{Q_2}{C_2} = \frac{31.8 \mu\text{C}}{12.0 \mu\text{F}} = \boxed{2.65 \text{ V}}$$

**P20.41** (a)  $\frac{1}{C_s} = \frac{1}{15.0} + \frac{1}{3.00}$

$$C_s = 2.50 \mu\text{F}$$

$$C_p = 2.50 + 6.00 = 8.50 \mu\text{F}$$

$$C_{eq} = \left( \frac{1}{8.50 \mu\text{F}} + \frac{1}{20.0 \mu\text{F}} \right)^{-1} = \boxed{5.96 \mu\text{F}}$$


(b)  $Q = C \Delta V = (5.96 \mu\text{F})(15.0 \text{ V}) = \boxed{89.5 \mu\text{C}}$  on  $20.0 \mu\text{F}$

$$\Delta V = \frac{Q}{C} = \frac{89.5 \mu\text{C}}{20.0 \mu\text{F}} = 4.47 \text{ V}$$

$$15.0 - 4.47 = 10.53 \text{ V}$$

$$Q = C \Delta V = (6.00 \mu\text{F})(10.53 \text{ V}) = \boxed{63.2 \mu\text{C}}$$
 on  $6.00 \mu\text{F}$

$$89.5 - 63.2 = \boxed{26.3 \mu\text{C}}$$
 on  $15.0 \mu\text{F}$  and  $3.00 \mu\text{F}$

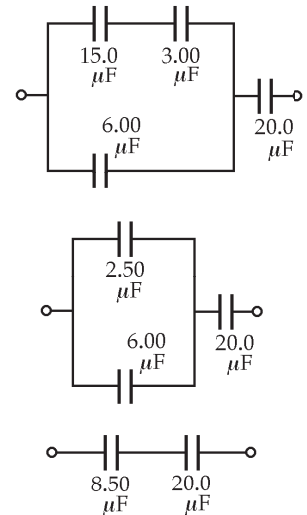

**FIG. P20.41**

**P20.43**  $C = \frac{Q}{\Delta V}$  so  $6.00 \times 10^{-6} = \frac{Q}{20.0}$

and  $Q = \boxed{120 \mu\text{C}}$


$Q_1 = 120 \mu\text{C} - Q_2$

and  $\Delta V = \frac{Q}{C}$ :  $\frac{120 - Q_2}{C_1} = \frac{Q_2}{C_2}$

or  $\frac{120 - Q_2}{6.00} = \frac{Q_2}{3.00}$

$(3.00)(120 - Q_2) = (6.00)Q_2$

$Q_2 = \frac{360}{9.00} = \boxed{40.0 \mu\text{C}}$   $Q_1 = 120 \mu\text{C} - 40.0 \mu\text{C} = \boxed{80.0 \mu\text{C}}$

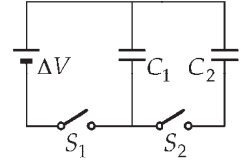

**FIG. P20.43**

**P20.48**  $U = \frac{1}{2} C \Delta V^2$

$\Delta V = \sqrt{\frac{2U}{C}} = \sqrt{\frac{2(300 \text{ J})}{30 \times 10^{-6} \text{ C/V}}} = \boxed{4.47 \times 10^3 \text{ V}}$

**P20.49**  $U = \frac{1}{2} C (\Delta V)^2$

The circuit diagram is shown at the right.



(a)  $C_p = C_1 + C_2 = 25.0 \mu\text{F} + 5.00 \mu\text{F} = 30.0 \mu\text{F}$

$U = \frac{1}{2} (30.0 \times 10^{-6}) (100)^2 = \boxed{0.150 \text{ J}}$

(b)  $C_s = \left( \frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = \left( \frac{1}{25.0 \mu\text{F}} + \frac{1}{5.00 \mu\text{F}} \right)^{-1} = 4.17 \mu\text{F}$

$U = \frac{1}{2} C (\Delta V)^2$

$\Delta V = \sqrt{\frac{2U}{C}} = \sqrt{\frac{2(0.150)}{4.17 \times 10^{-6}}} = \boxed{268 \text{ V}}$

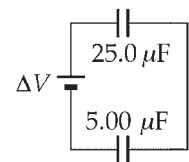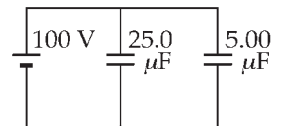

**FIG. P20.49**

**P20.53** (a)

$C = \frac{\kappa \epsilon_0 A}{d} = \frac{2.10 (8.85 \times 10^{-12} \text{ F/m}) (1.75 \times 10^{-4} \text{ m}^2)}{4.00 \times 10^{-5} \text{ m}} = 8.13 \times 10^{-11} \text{ F} = \boxed{81.3 \text{ pF}}$

$$(b) \quad \Delta V_{\max} = E_{\max} d = (60.0 \times 10^6 \text{ V/m})(4.00 \times 10^{-5} \text{ m}) = \boxed{2.40 \text{ kV}}$$

**P20.59** The energy transferred is  $T_{\text{ET}} = \frac{1}{2} Q \Delta V = \frac{1}{2} (50.0 \text{ C})(1.00 \times 10^8 \text{ V}) = 2.50 \times 10^9 \text{ J}$

and 1% of this (or  $\Delta E_{\text{int}} = 2.50 \times 10^7 \text{ J}$ ) is absorbed by the tree. If  $m$  is the amount of water boiled away,

then

$$\Delta E_{\text{int}} = m(4186 \text{ J/kg} \cdot ^\circ\text{C})(100^\circ\text{C} - 30.0^\circ\text{C}) + m(2.26 \times 10^6 \text{ J/kg}) = 2.50 \times 10^7 \text{ J}$$

giving  $m = \boxed{9.79 \text{ kg}}$ .